

On-chip superconducting resonators


Gergő Fülöp
RF seminar
2019-03-11

From the previous episode ...

- Coaxial cables
- Attenuators
- Directional coupler
- Bias tee
- Isolator/circulator
- Filters
- Amplifiers
- DC block


- Mixer
- (Power detector)
- Multiplexer
 - Diplexer

Oxford Triton dilfridge

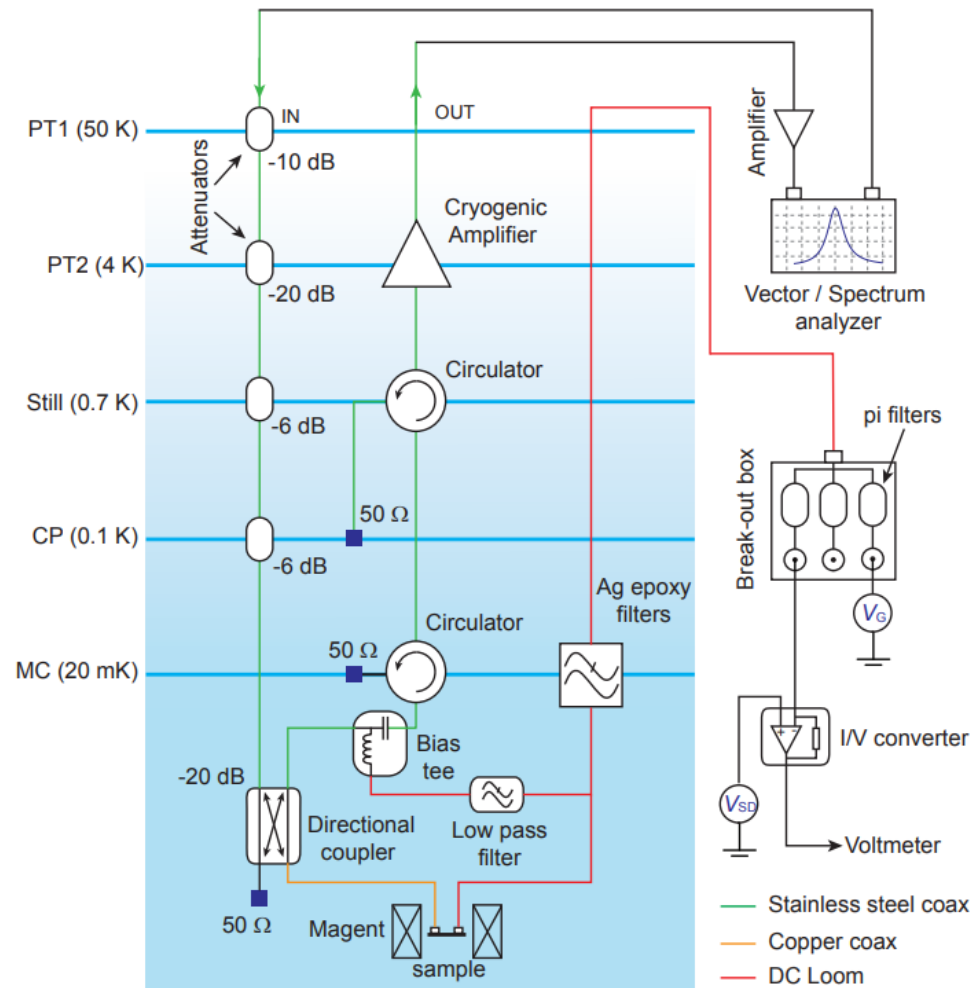

V. Ranjan, PhD thesis

What is on the chip?

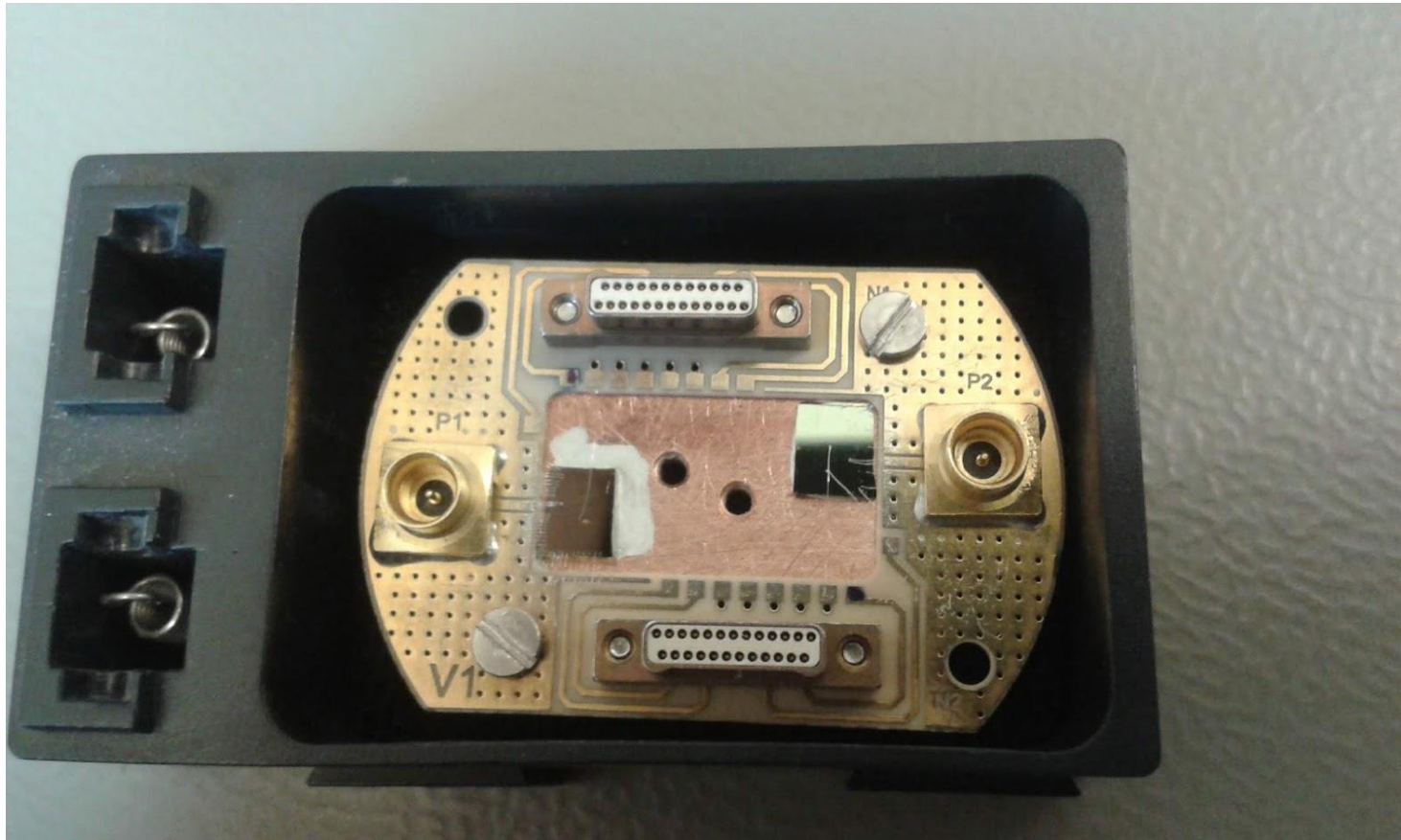


Overview

- Distributed resonators
 - Transmission lines
 - CPWs
 - striplines
 - CPW resonators
 - Quarter-wave resonator
 - Half-wave resonator
 - Stub tuner
 - Loss
 - Ground plane
- Lumped element resonators
- Coupling to devices
- Kinetic inductance
 - Stripline resonators
 - High-impedance resonators
- Remarks

Transmission lines

- Distributed model

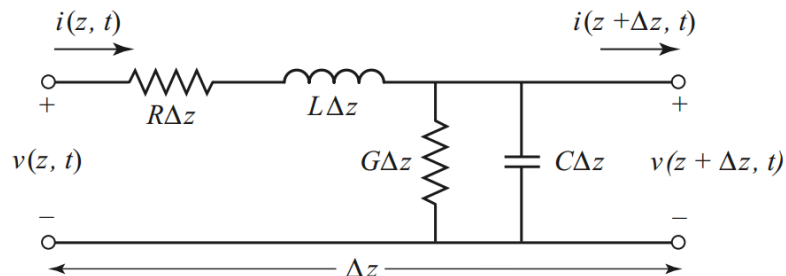


Propagation constant:

$$\gamma = \alpha + j\beta$$

$$\frac{V_o^+}{I_o^+} = Z_0$$
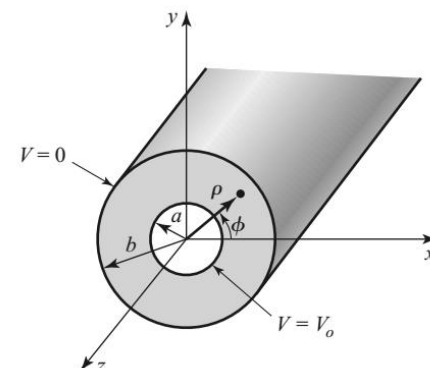
$$Z_0 = \frac{R + j\omega L}{\gamma} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$




- Lossless TL

$$\gamma = \alpha + j\beta = j\omega\sqrt{LC},$$

$$Z_0 = \sqrt{\frac{L}{C}},$$


- Reflection

- From the end of the TL

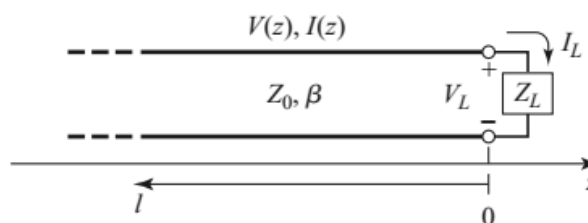

$$\Gamma = \frac{V_o^-}{V_o^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$


- Interfaces

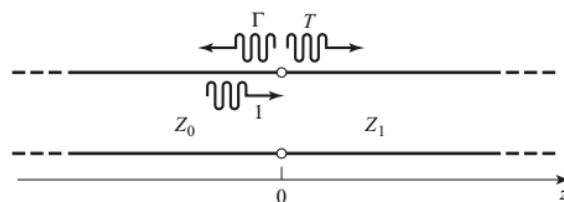

$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

Transmission lines

- Coplanar waveguide

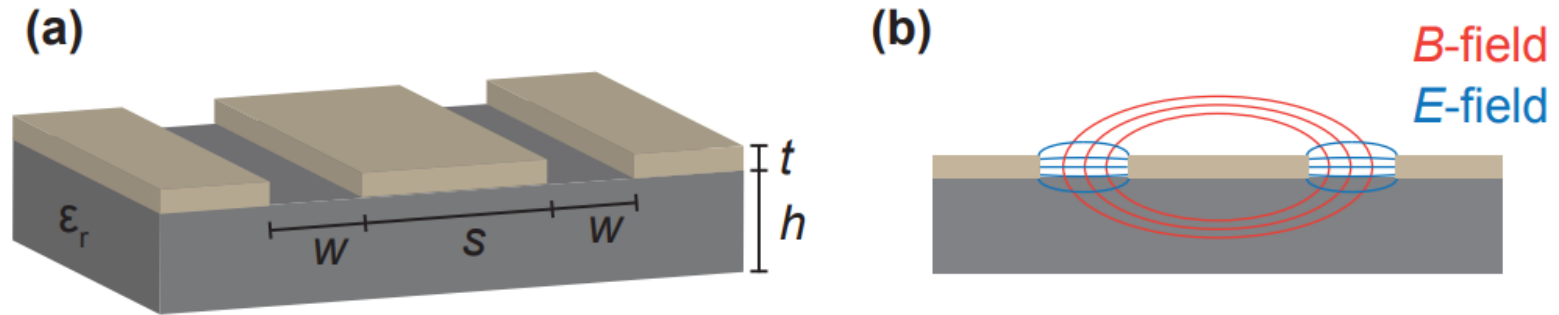

- Characteristic impedance


$$\epsilon_{\text{eff}} = 1 + \frac{\epsilon_r - 1}{2} \cdot \frac{K(k_1)K(k'_0)}{K(k'_1)K(k_0)}$$

$$k_0 = \frac{s}{s + 2w}$$

$$k'_0 = \sqrt{1 - k_0^2}$$


$$k_1 = \frac{\sinh(\pi s/4h)}{\sinh(\pi(s + 2w)/4h)}$$

$$k'_1 = \sqrt{1 - k_1^2}$$

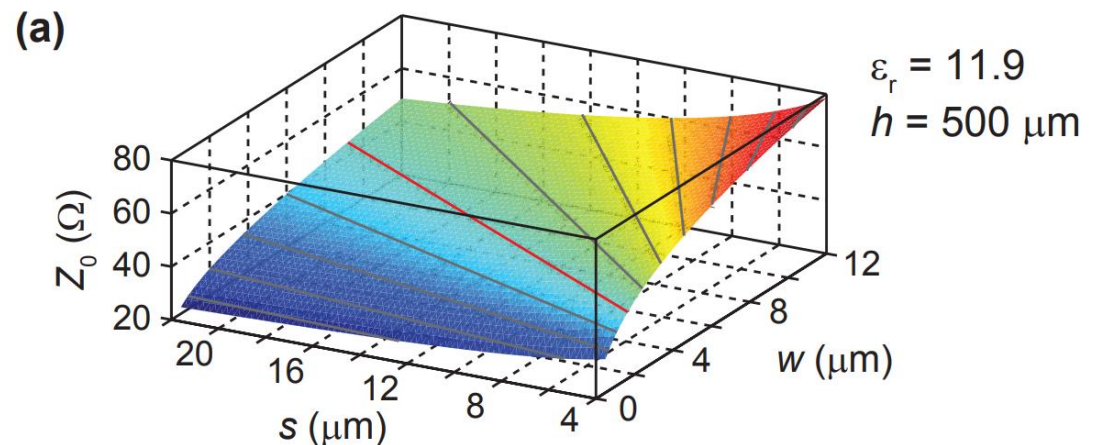


Transmission lines

- Stripline / microstrip

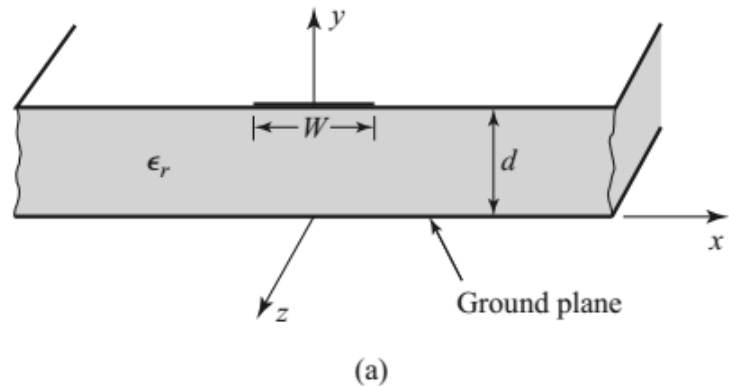
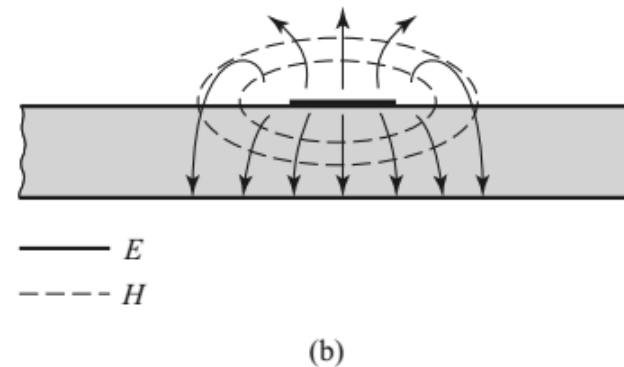
$$\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \frac{1}{\sqrt{1 + 12d/W}}$$





- Characteristic impedance



$$Z_0 = \begin{cases} \frac{60}{\sqrt{\epsilon_e}} \ln \left(\frac{8d}{W} + \frac{W}{4d} \right) & \text{for } W/d \leq 1 \\ \frac{120\pi}{\sqrt{\epsilon_e} [W/d + 1.393 + 0.667 \ln (W/d + 1.444)]} & \text{for } W/d \geq 1. \end{cases}$$

Quarter-wave CPW resonator

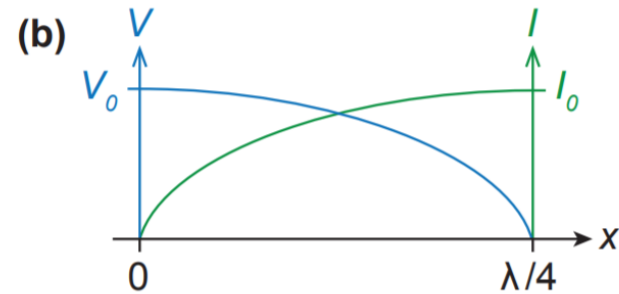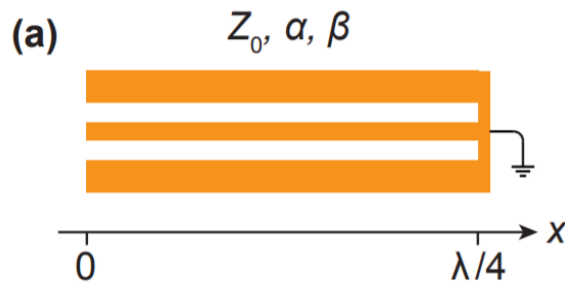- Model
 - CPW with open end + shorted end



- Realization $l \approx \lambda/4$

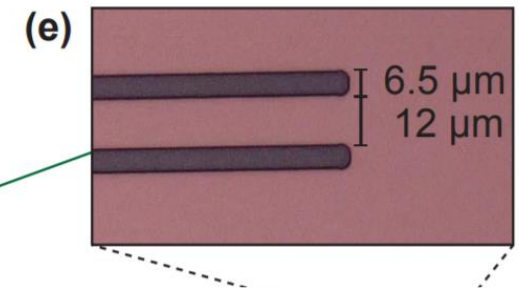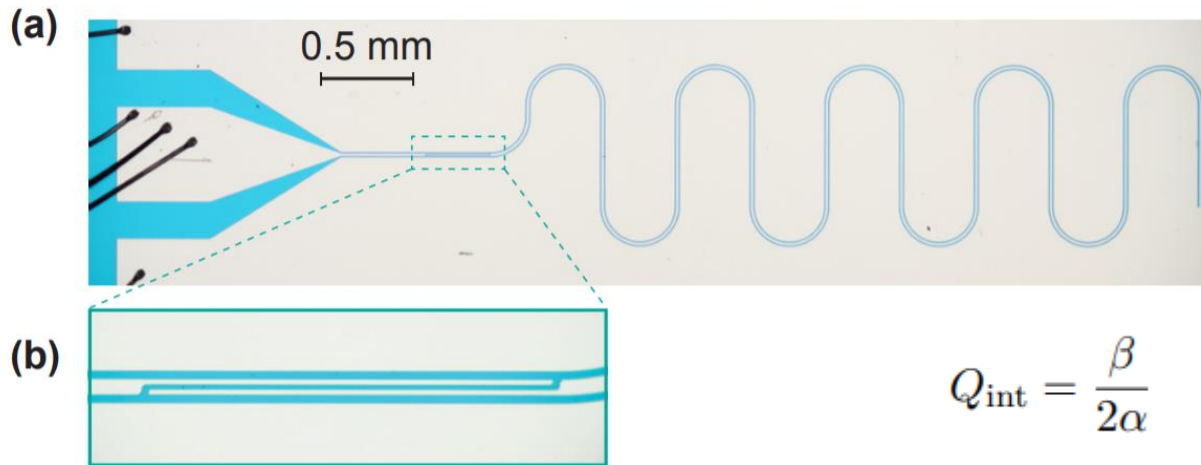

$$Q = \omega \cdot \frac{\text{energy stored in resonator}}{\text{power dissipated}}$$

$$Q_{\text{int}} = \frac{\beta}{2\alpha}$$

$$Q_c = \frac{1}{8\pi (Z_0 f C_c)^2}$$


$$\frac{1}{Q_l} = \frac{1}{Q_i} + \frac{1}{Q_c}$$

Quality factor

- Definition

$$Q = \omega \frac{\text{average energy stored}}{\text{energy loss/second}}$$

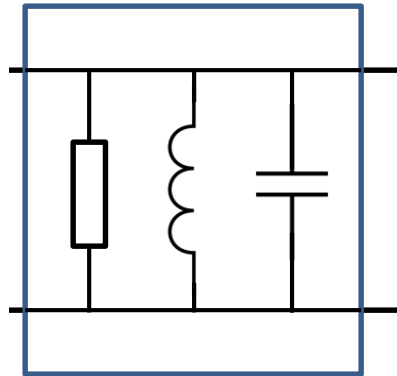- Internal, intrinsic, external, loaded, total [...] Q



$$Q_0 = \omega_0 RC = \frac{R}{\omega_0 L}$$

$$Q_e = \frac{R_L}{\omega_0 L}$$

$$\frac{1}{Q_l} = \frac{1}{Q_0} + \frac{1}{Q_e}$$


- Determination

$$Q_l = \frac{f_0}{\text{FWHM}}$$


$$\kappa_L = \kappa_i + \kappa_c$$

Quarter-wave CPW resonator

- 14 nm NbTiN film, out-of-plane B field

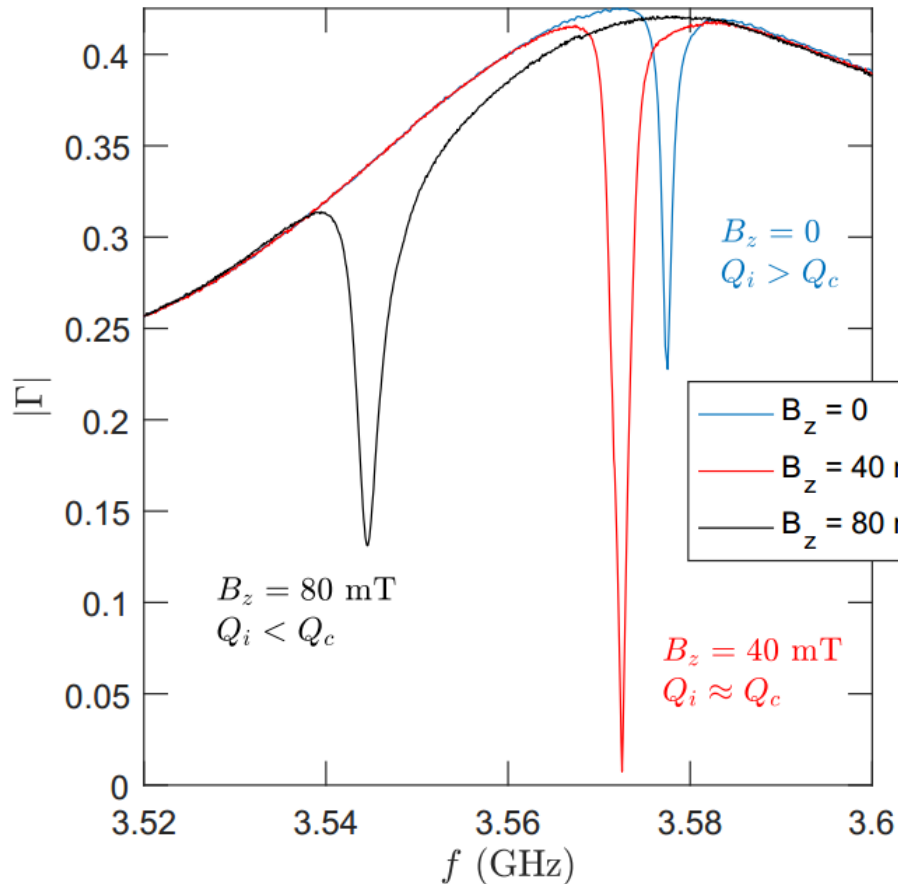


(a) B_z -dependence, magnitude traces

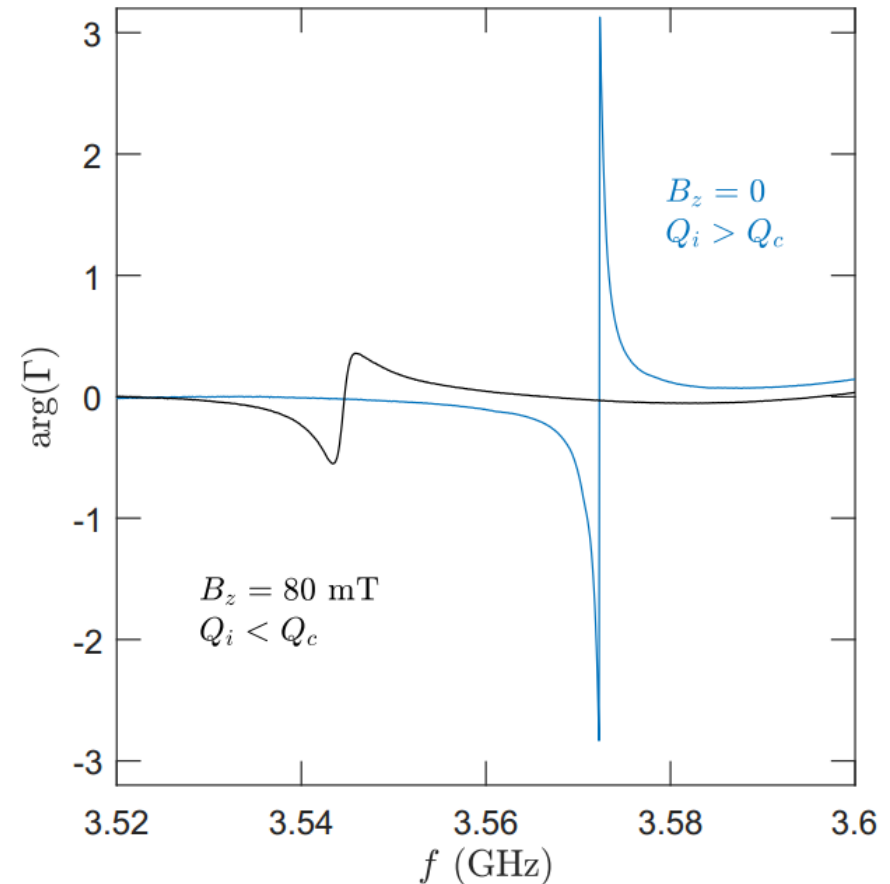


(b) B_z -dependence, phase traces

Quarter-wave CPW resonator

- 14 nm NbTiN film, in-plane B field

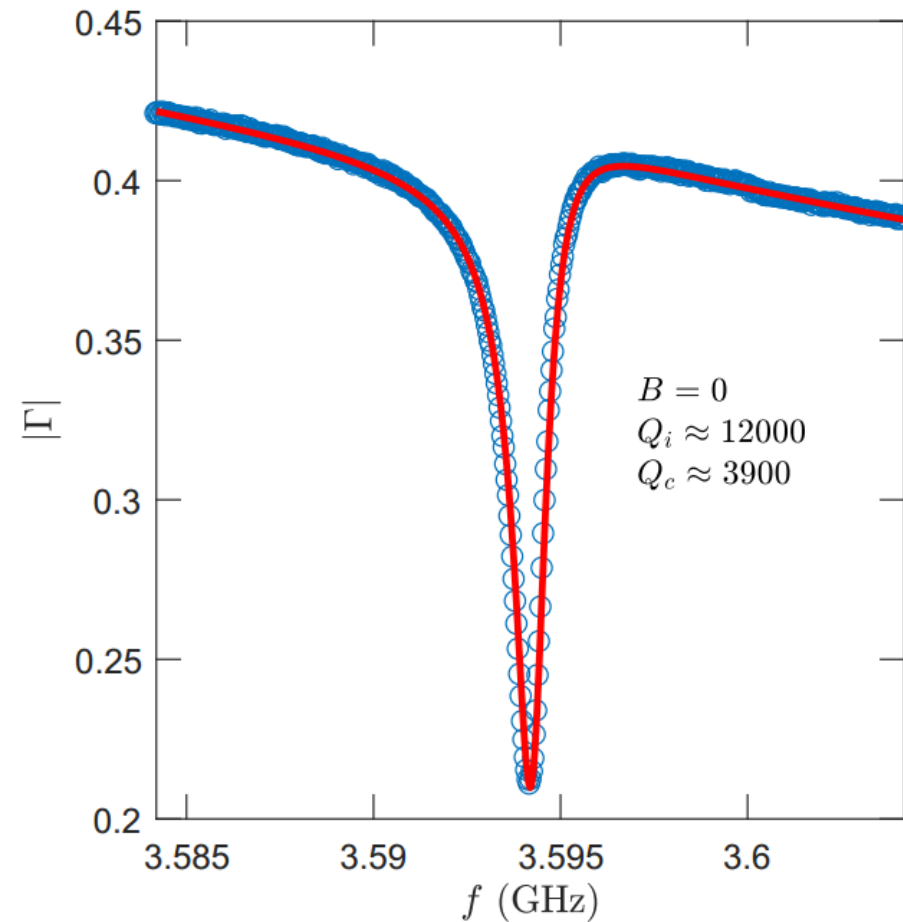



(a) Fitted resonance curve, $B = 0$

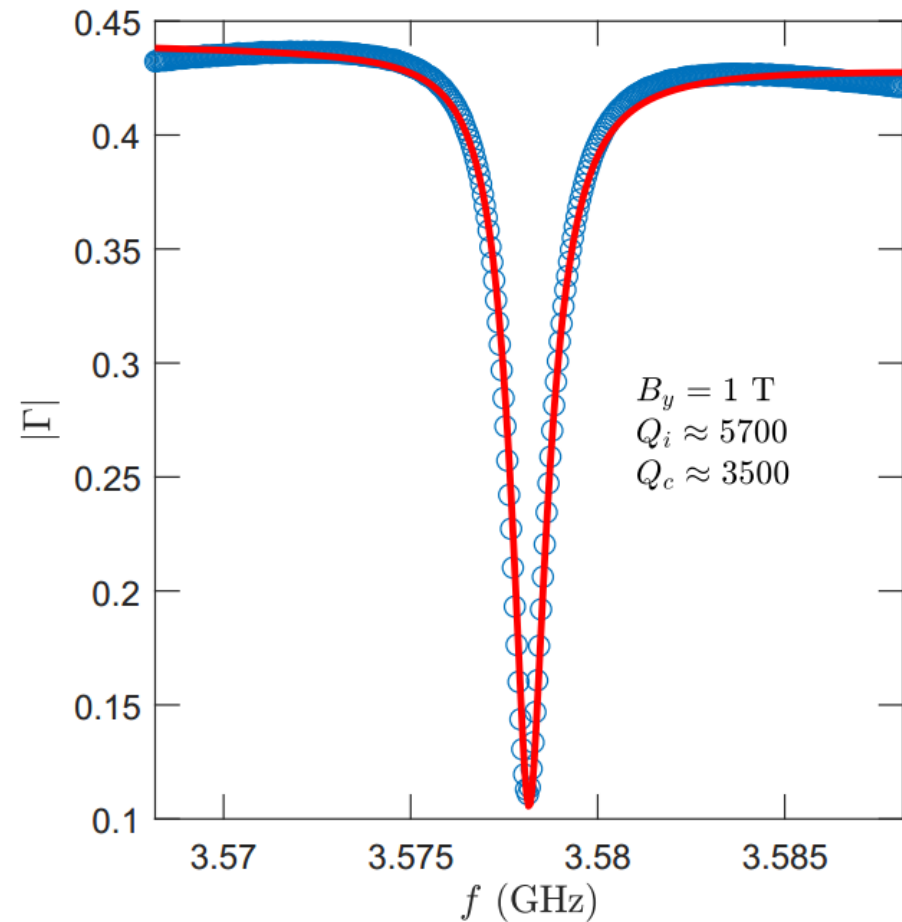

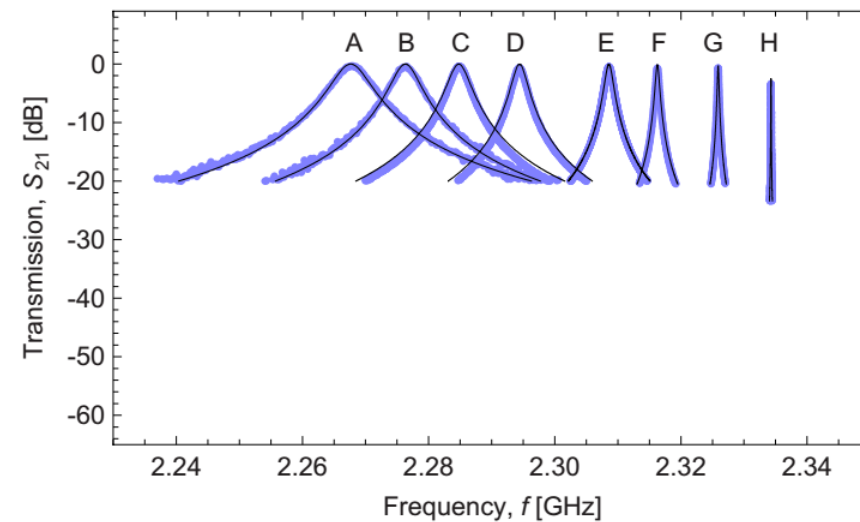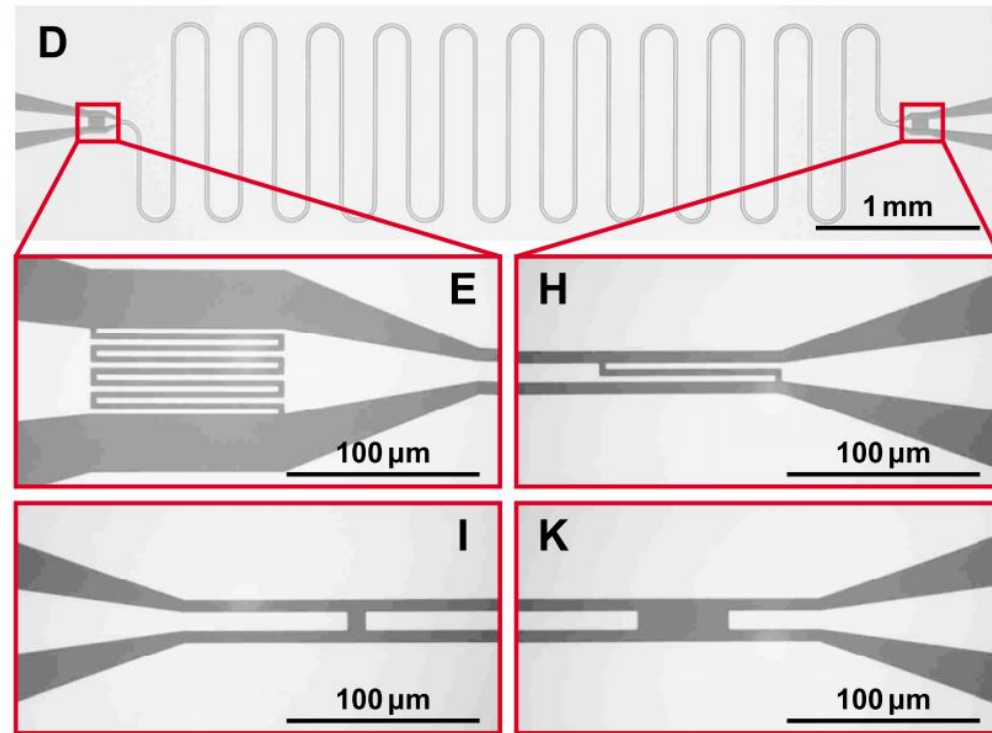(b) Fitted resonance curve, $B_y = 1$ T

Half-wave CPW resonator

- Capacitor – CPW – Capacitor
 - Fabry-Perot cavity




J. Appl. Phys. 104, 113904 (2008);

Half-wave CPW resonator

- Capacitor – CPW – Capacitor


Distributed model

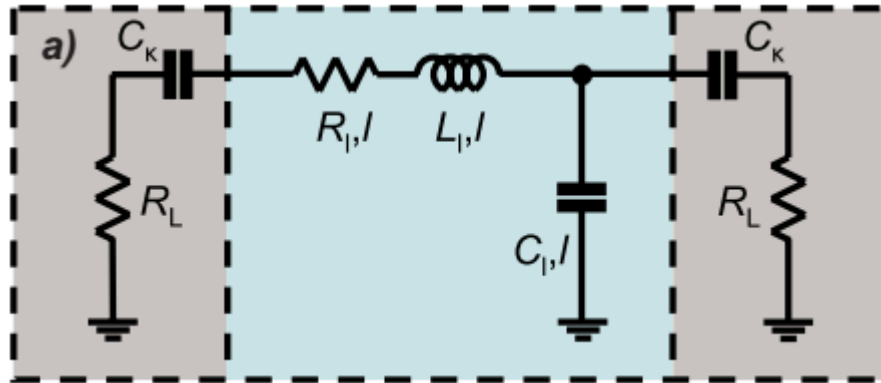

$$Z_{TL} = Z_0 \frac{1 + i \tan \beta l \tanh \alpha l}{\tanh \alpha l + i \tan \beta l},$$

$$\approx \frac{Z_0}{\alpha l + i \frac{\pi}{\omega_0} (\omega - \omega_n)}.$$

Lumped element model

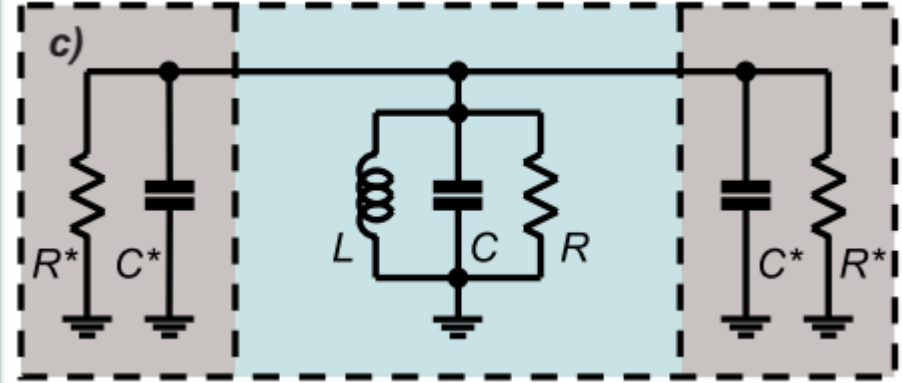


$$Z_{LCR} = \left(\frac{1}{i\omega L_n} + i\omega C + \frac{1}{R} \right)^{-1},$$

$$\approx \frac{R}{1 + 2iRC(\omega - \omega_n)},$$

J. Appl. Phys. 104, 113904 (2008);

Half-wave CPW resonator

- Capacitor – CPW – Capacitor

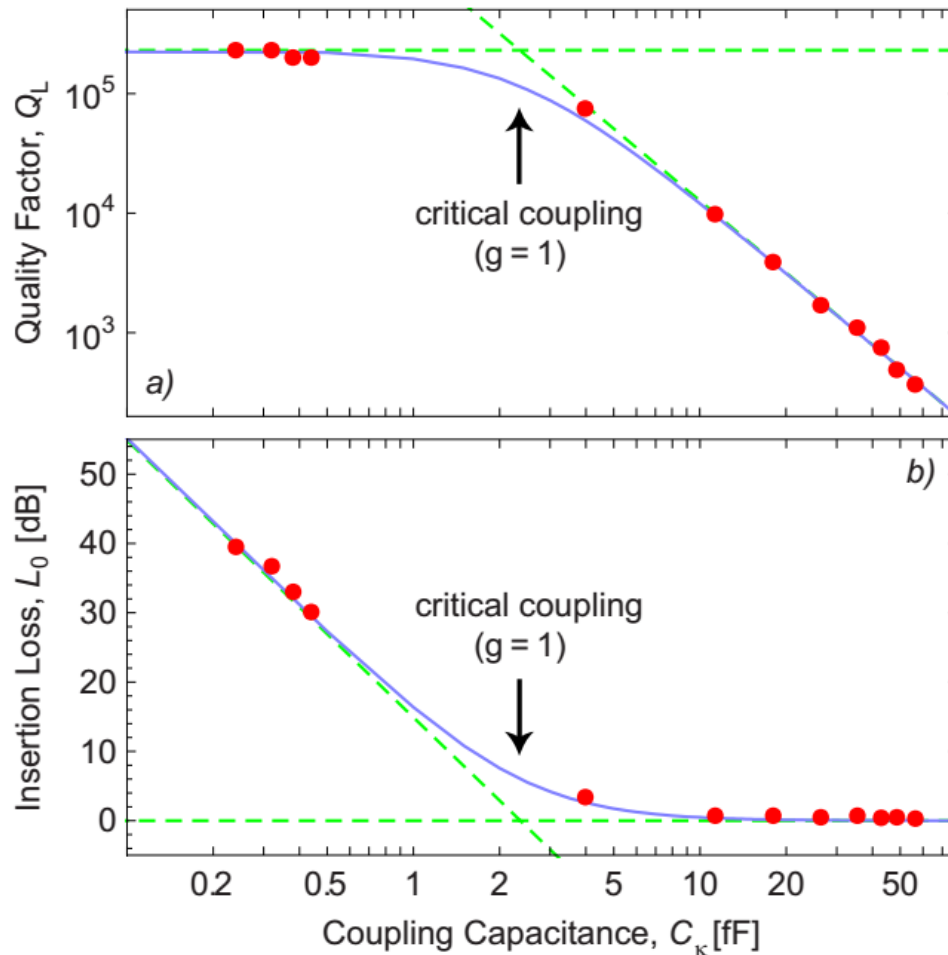

$$Q_{\text{int}} = \omega_n RC = \frac{n\pi}{2\alpha l},$$

$$Q_{\text{ext}} = \frac{\omega_n R^* C}{2}.$$


$$L_0 = -20 \log\left(\frac{g}{g+1}\right) \text{dB}$$

$$g = Q_{\text{int}} / Q_{\text{ext}}$$

J. Appl. Phys. 104, 113904 (2008);

CPW Stub tuner

- Stub tuner

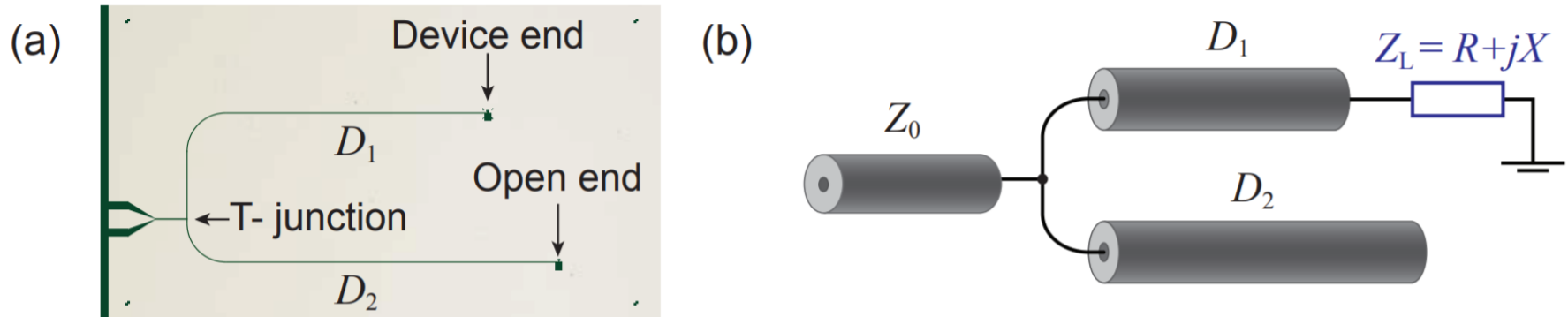


- Measure admittance (resistance, capacitance)
- Measure noise

V. Ranjan, PhD Thesis

- Compact form



- Meander
- Bond bridges

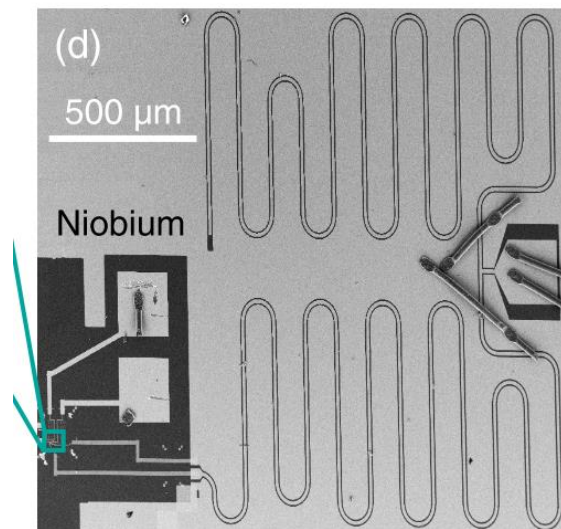

T. Hasler, PhD Thesis






Lumped element resonators

- Simple LC

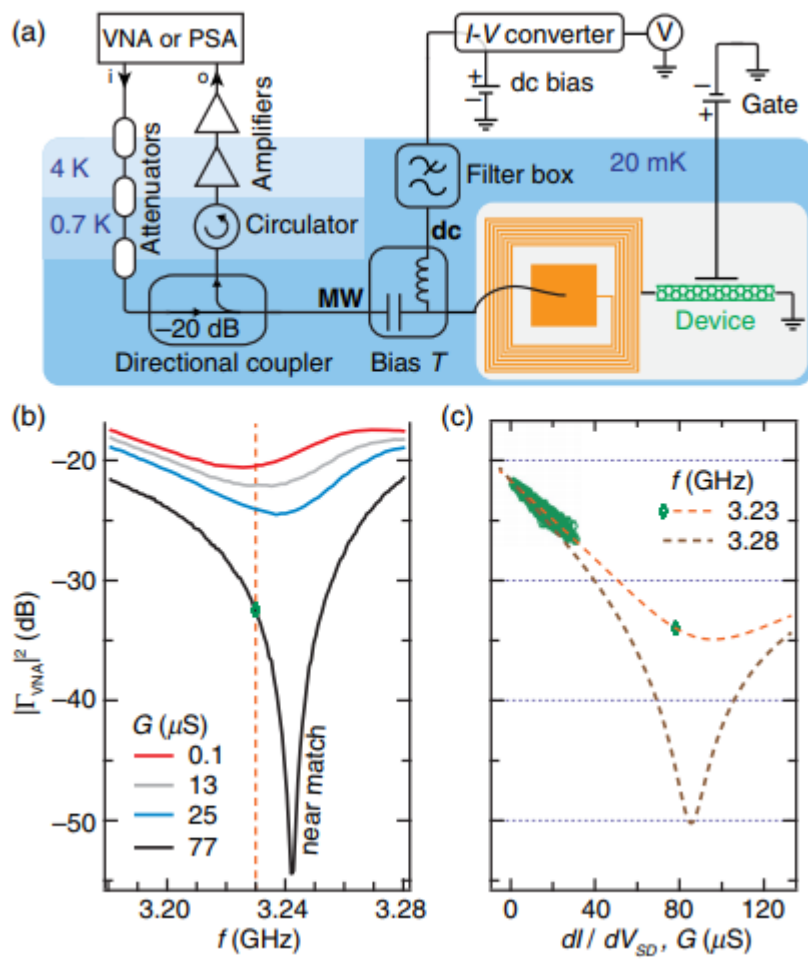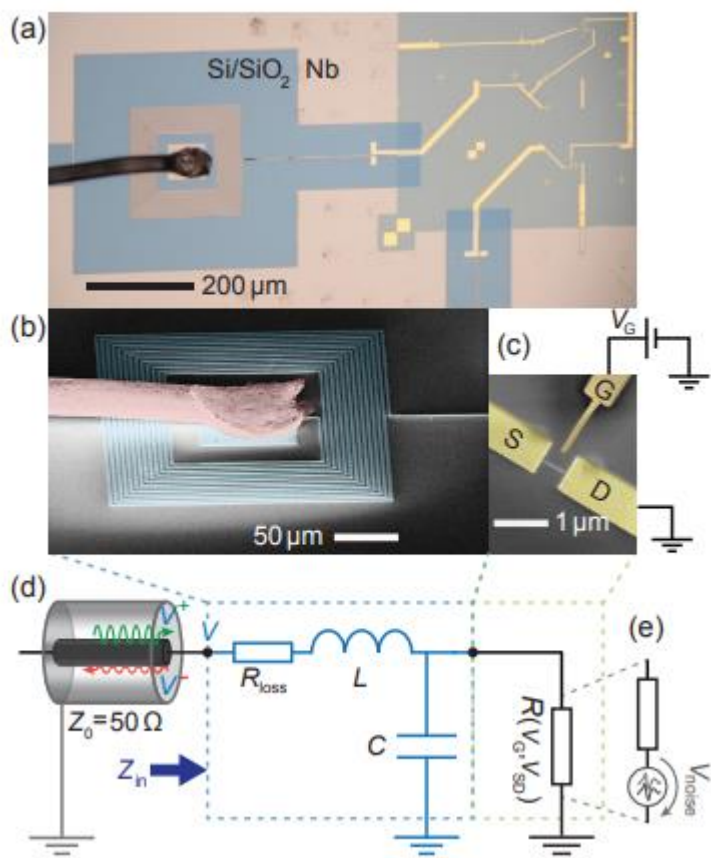

Feedline

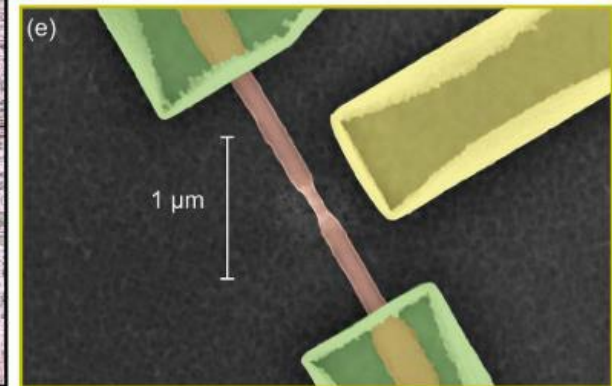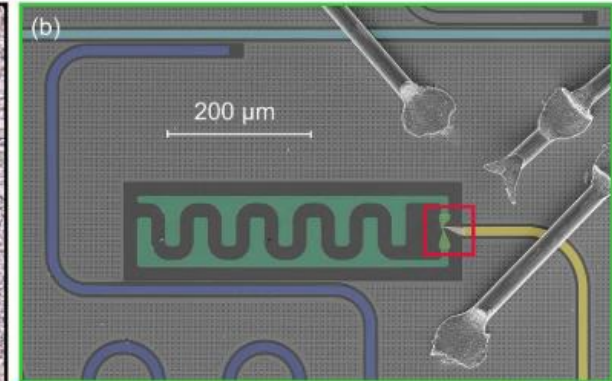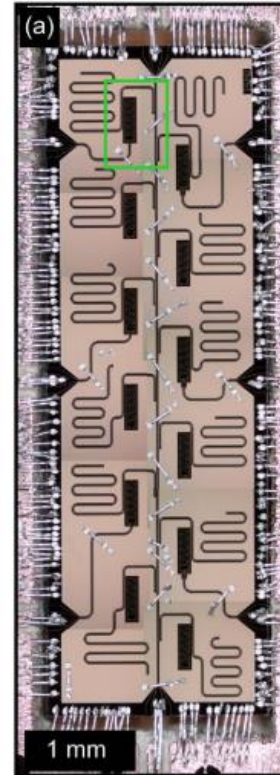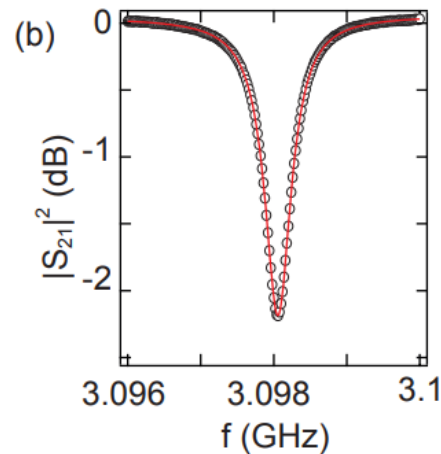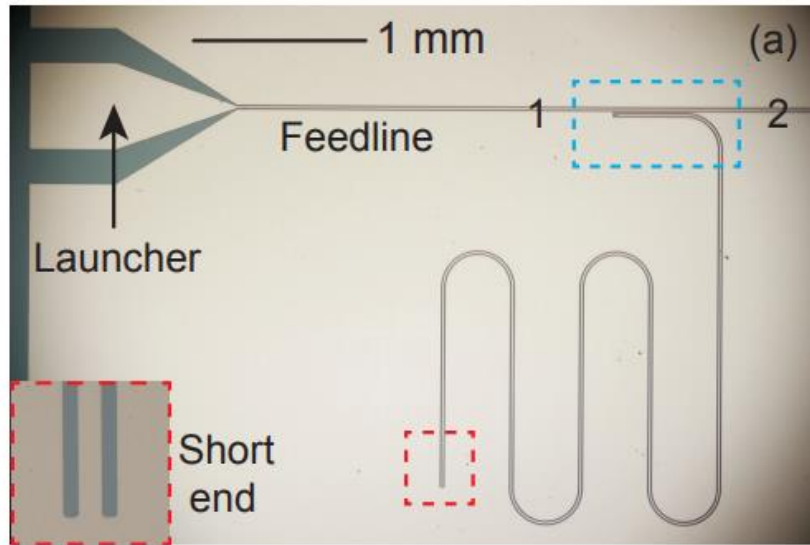
- Feedline with “hanging” quarter-wave resonators




Phys. Rev. Lett. **120**, 100502 (2018)

- Conductor losses
 - Superconducting film
 - Dissipation for non-zero frequencies
- TLS
 - Mostly at interfaces
 - Nitrides are better (?)
- Common materials:
 - Oxideless Si wafer
 - Sapphire wafer (transparent!)
 - Kapton substrate (flexible, for break junctions)
 - E.g. Coherent manipulation of Andreev Bound States in an atomic contact, Camille Janvier

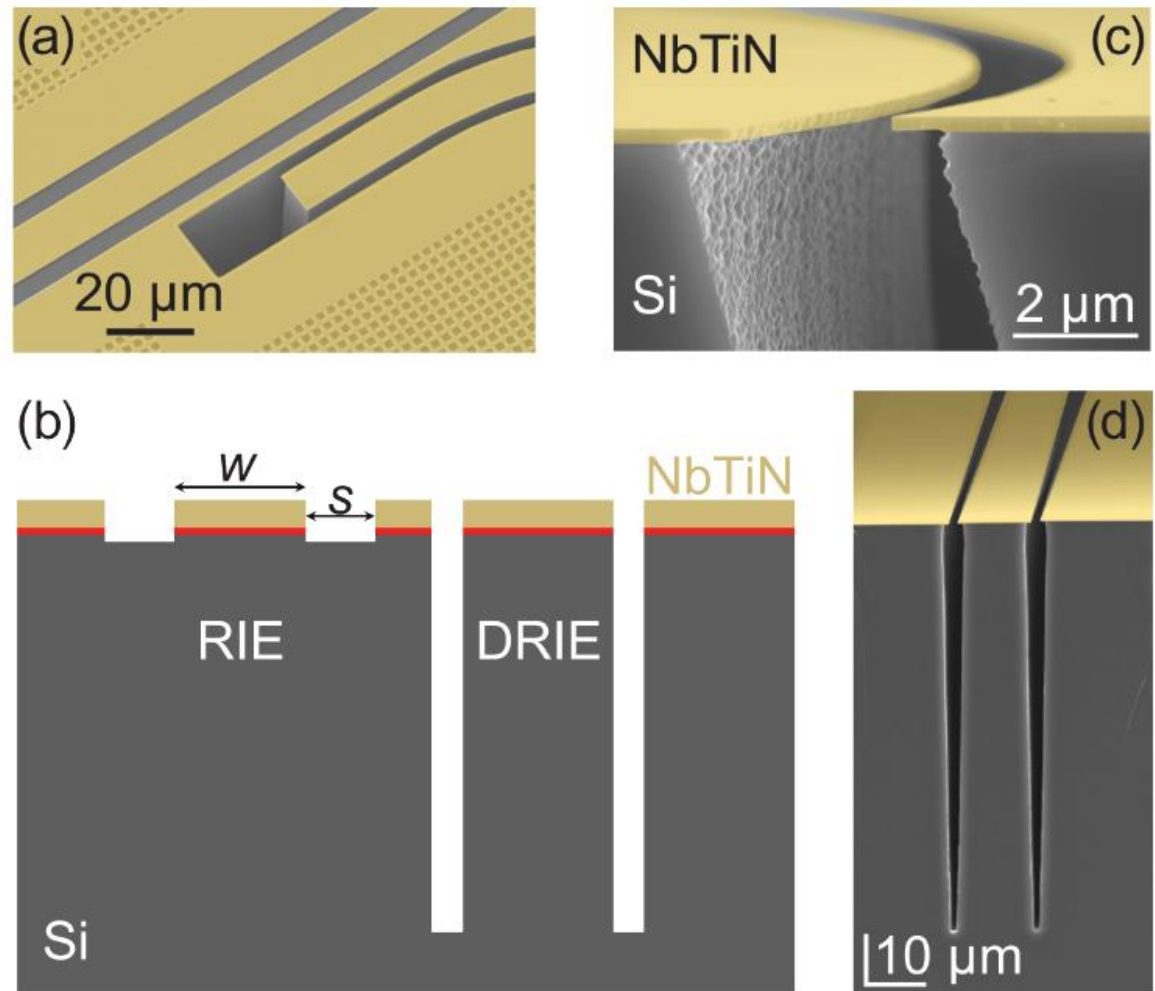
- Annealing
- Trenches
- Holes in the film
 - Vortex pinning
 - Suppress spurious modes



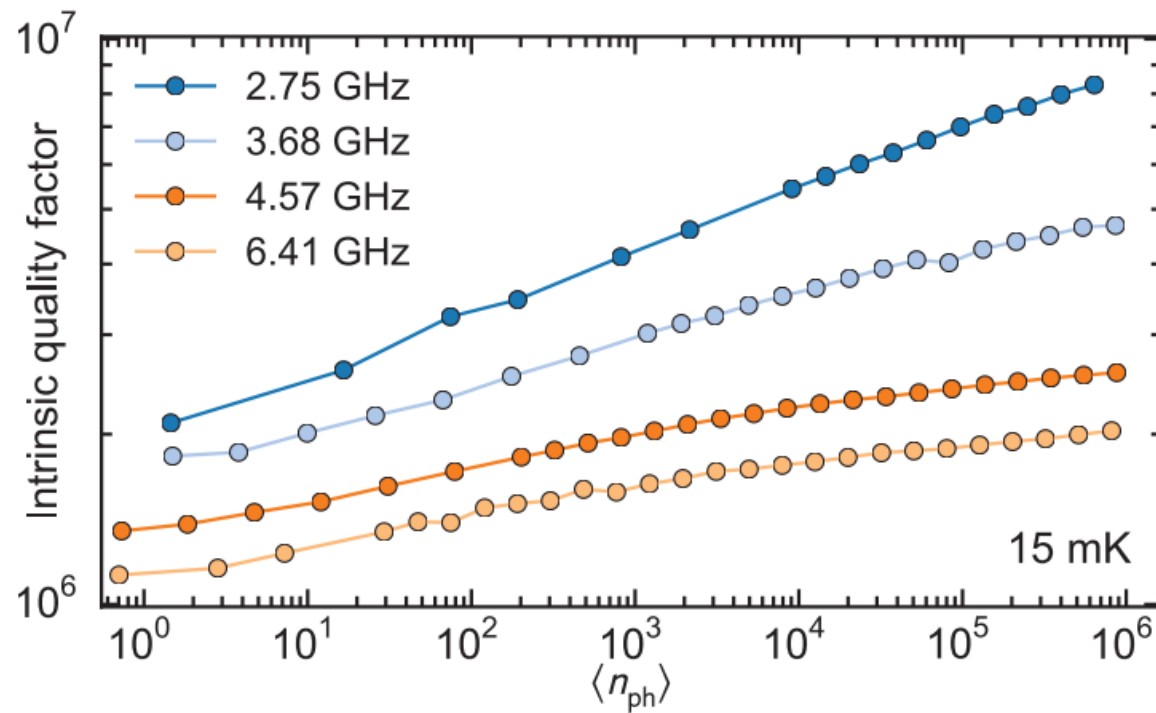- Annealing
- Trenches
- Holes in the film
 - Vortex pinning
 - Suppress spurious modes




Appl. Phys. Lett. **106**, 182601 (2015)

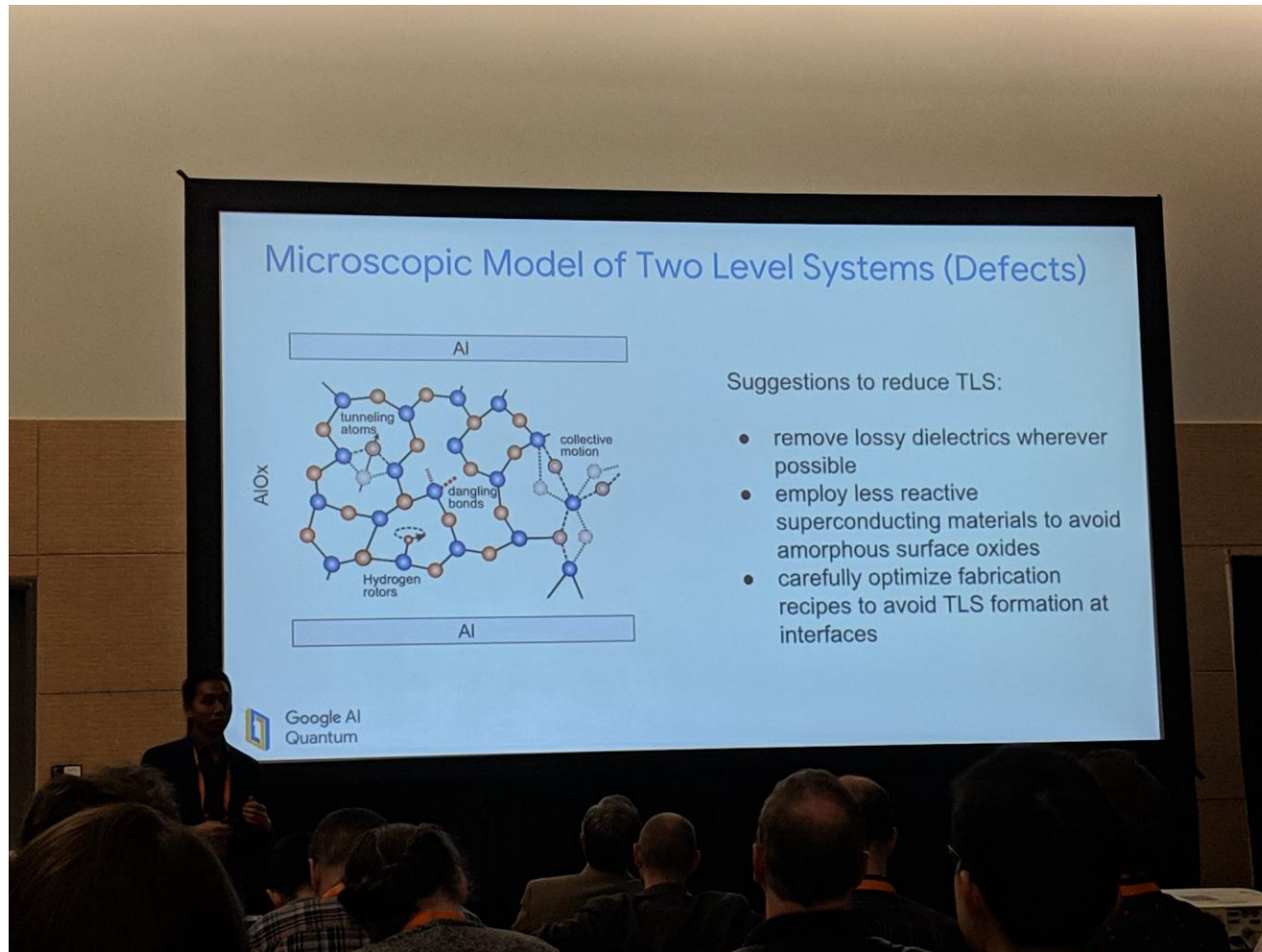


<https://twitter.com/quantumVerd/status/1103749781015482369>

Resonator-device coupling

- Galvanic

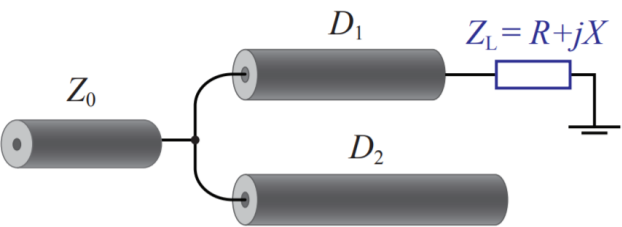


V. Ranjan, PhD Thesis

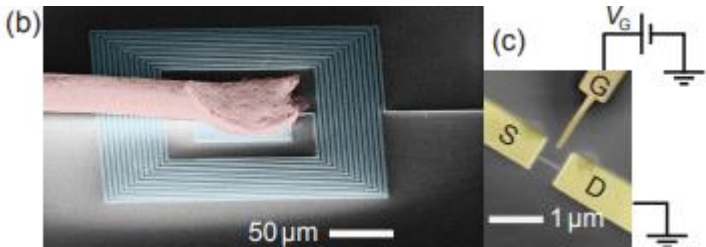


PHYSICAL REVIEW APPLIED 8, 054006 (2017)

- Capacitive

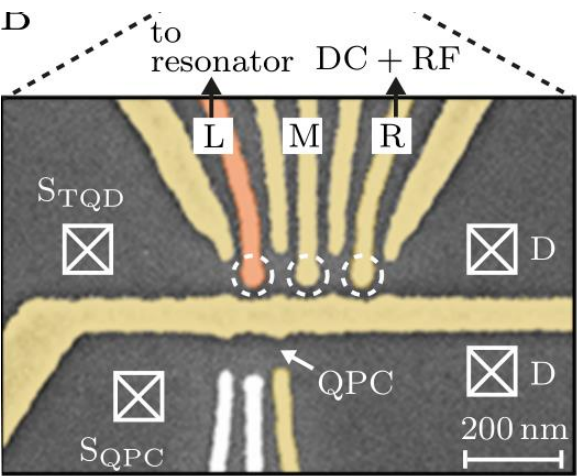


Nature 560, 179–184 (2018)

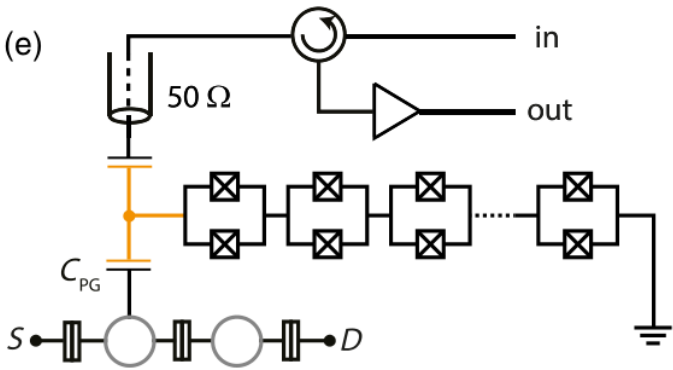


PHYS. REV. X 7, 011030 (2017)

Resonator-device coupling

- Inductive

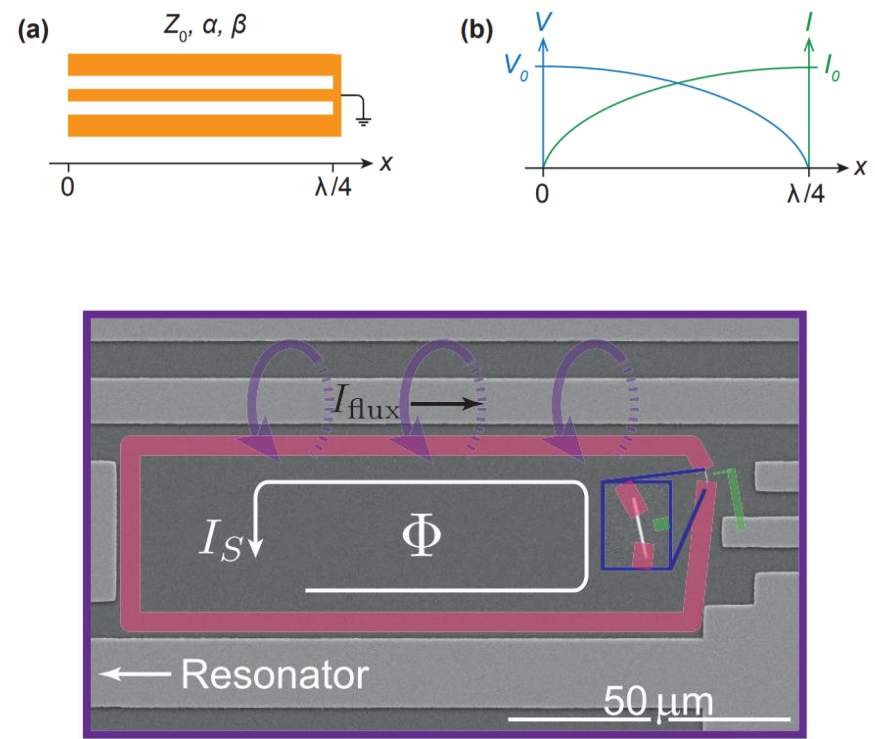

R. Haller

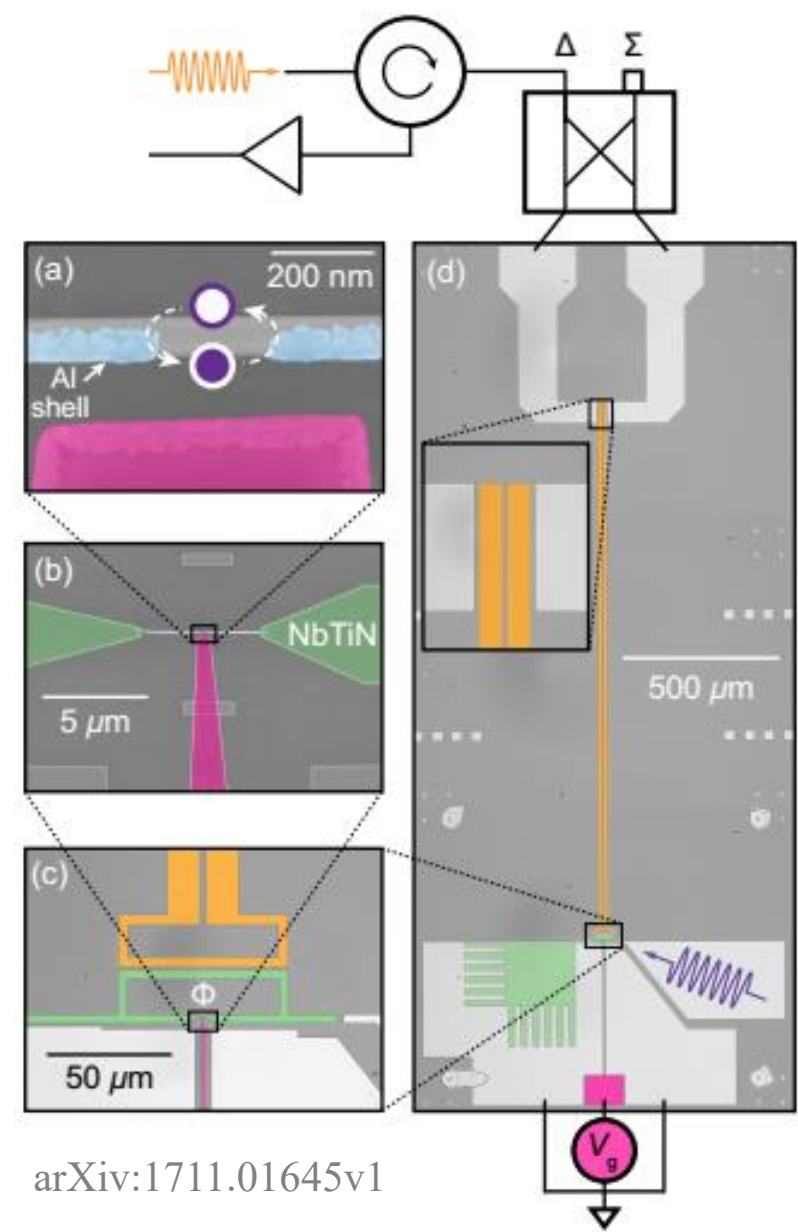

arXiv:1711.01645v1

Kinetic inductance

- Drude model

$$\sigma = \frac{ne^2\tau}{m(1+i\omega\tau)} = \frac{ne^2\tau}{m(1+\omega^2\tau^2)} - i\frac{ne^2\omega\tau^2}{m(1+\omega^2\tau^2)}$$

- Low frequencies or short collision time $\rightarrow$ imaginary part is negligible

- Kinetic energy of Cooper pairs

- Strip of length l , cross section A

$$\frac{1}{2}(2mv^2)(n_slA) = \frac{1}{2}L_K I^2$$

$$L_K = \left(\frac{m}{2n_se^2} \right) \left(\frac{l}{A} \right)$$

- Scales like resistance!

- From BCS theory:

$$L_k^\square(0) = \frac{\hbar R_N^\square}{\pi \Delta_0}$$

$$\Delta_0 = 2.08k_B T_c$$


- Tunability:

- Temperature
 - Current

arXiv:1802.01723v1

A.J. Annunziata *et al.*, "Tunable superconducting nanoinductors," *Nanotechnology* **21**, 445202 (2010)

Kinetic inductance

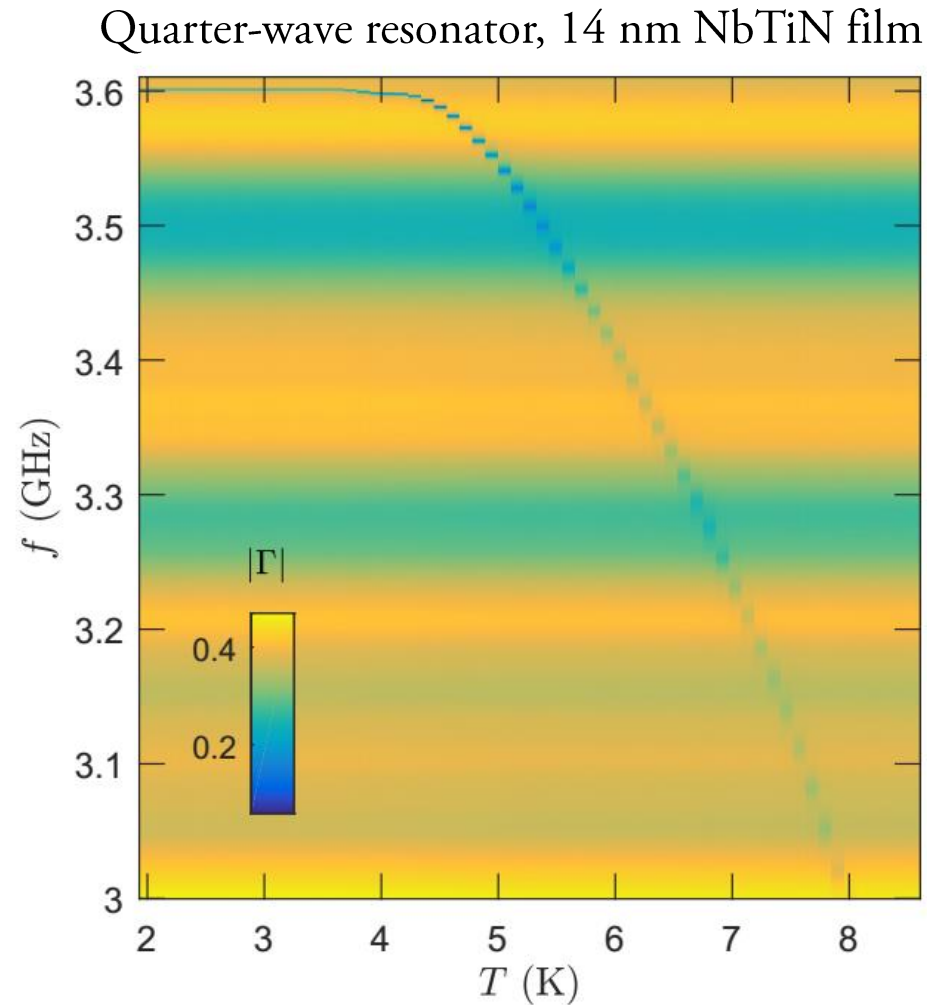


- Tunability:
 - Temperature
 - Current

arXiv:1802.01723v1

A.J. Annunziata *et al.*, "Tunable superconducting nanoinductors," *Nanotechnology* **21**, 445202 (2010)

Kinetic inductance, high-Z resonators

- Motivation
 - 1D cavity

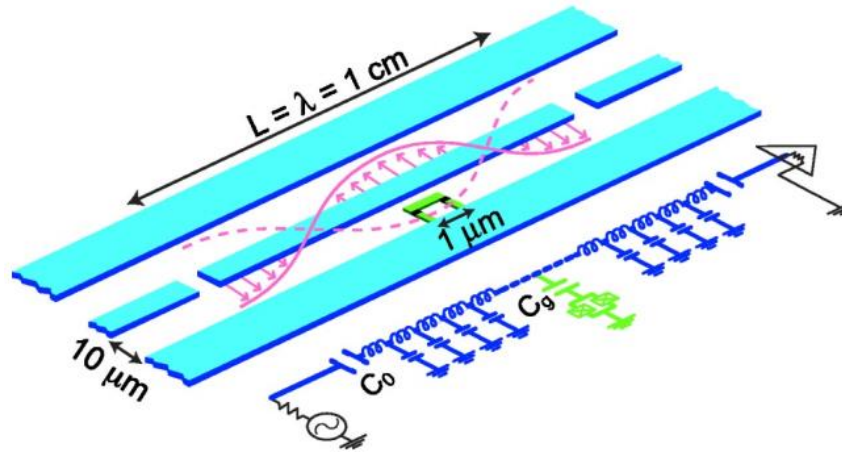

- Small volume / distance → large E field

$$V_{\text{rms}}^0 \sim \sqrt{\hbar \omega_r / cL}$$

10 GHz ($\hbar \nu / k_B \sim 0.5$ K)

10 μm gap

$$V_{\text{rms}} \sim 2 \mu\text{V}$$



$$\mathcal{E}_{\text{rms}} \sim 0.2 \text{ V/m}$$

- Coupling strength to qubits
- Strong coupling regime

$$g \gg \kappa, \gamma$$

Kinetic inductance, high-Z resonators

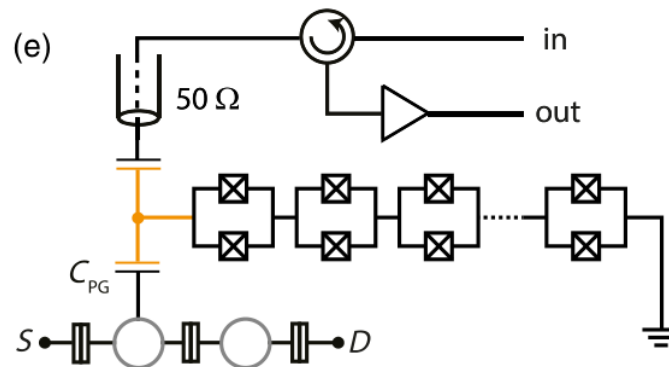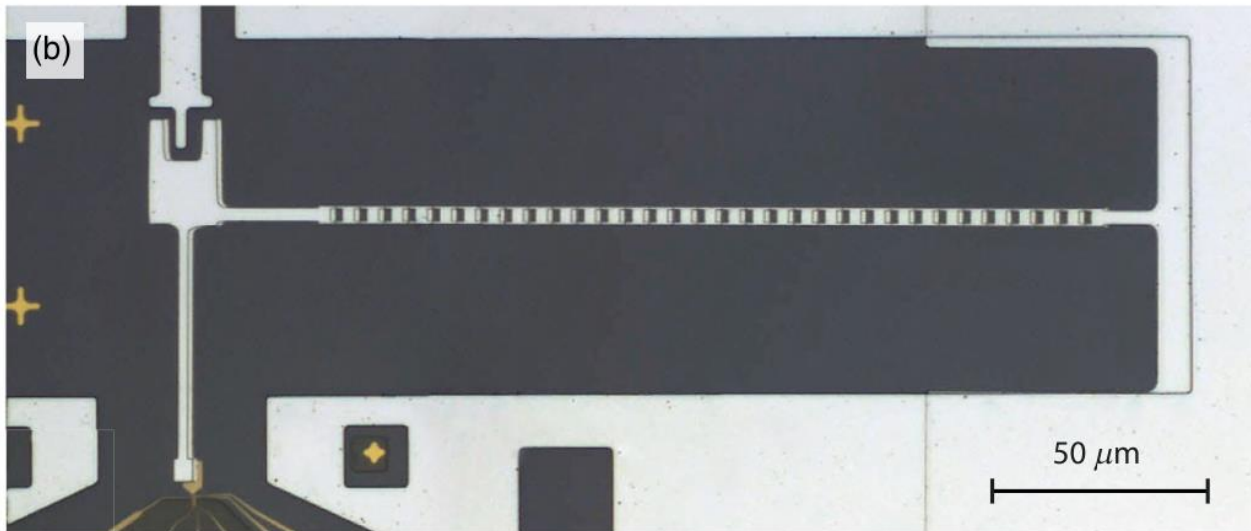
- Realization in CPW geometry
 - SQUID array (32 SQUIDs)
 - $Z = 1.3 - 1.8 \text{ k}\Omega$
 - Tunable with B field



PHYS. REV. X 7, 011030 (2017)


Kinetic inductance, high-Z resonators

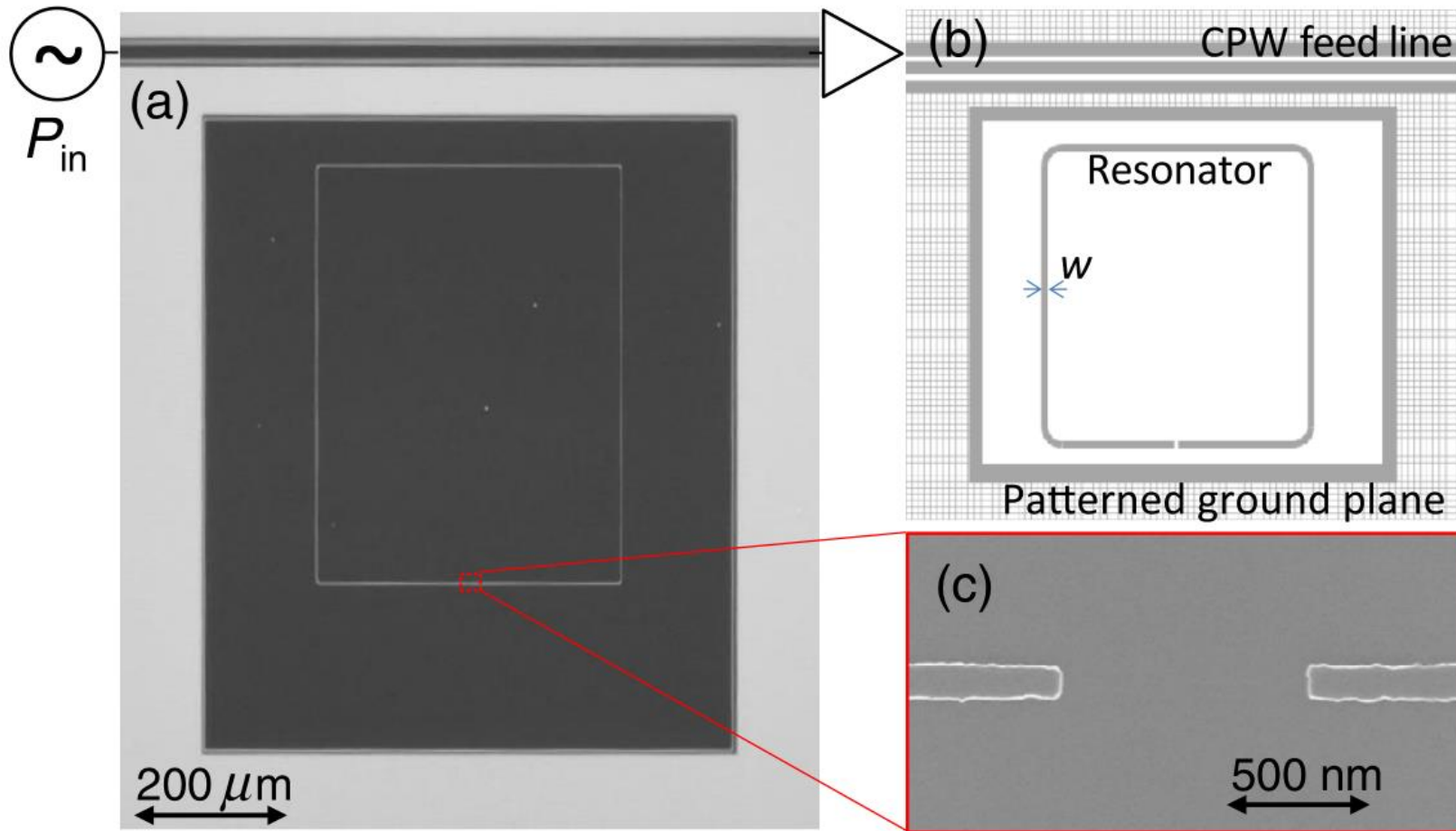- Realization: CPW feedline + stripline
 - NbTiN, $Z = 4 \text{ k}\Omega$



Kinetic inductance, high-Z resonators


- Realization: CPW feedline + stripline

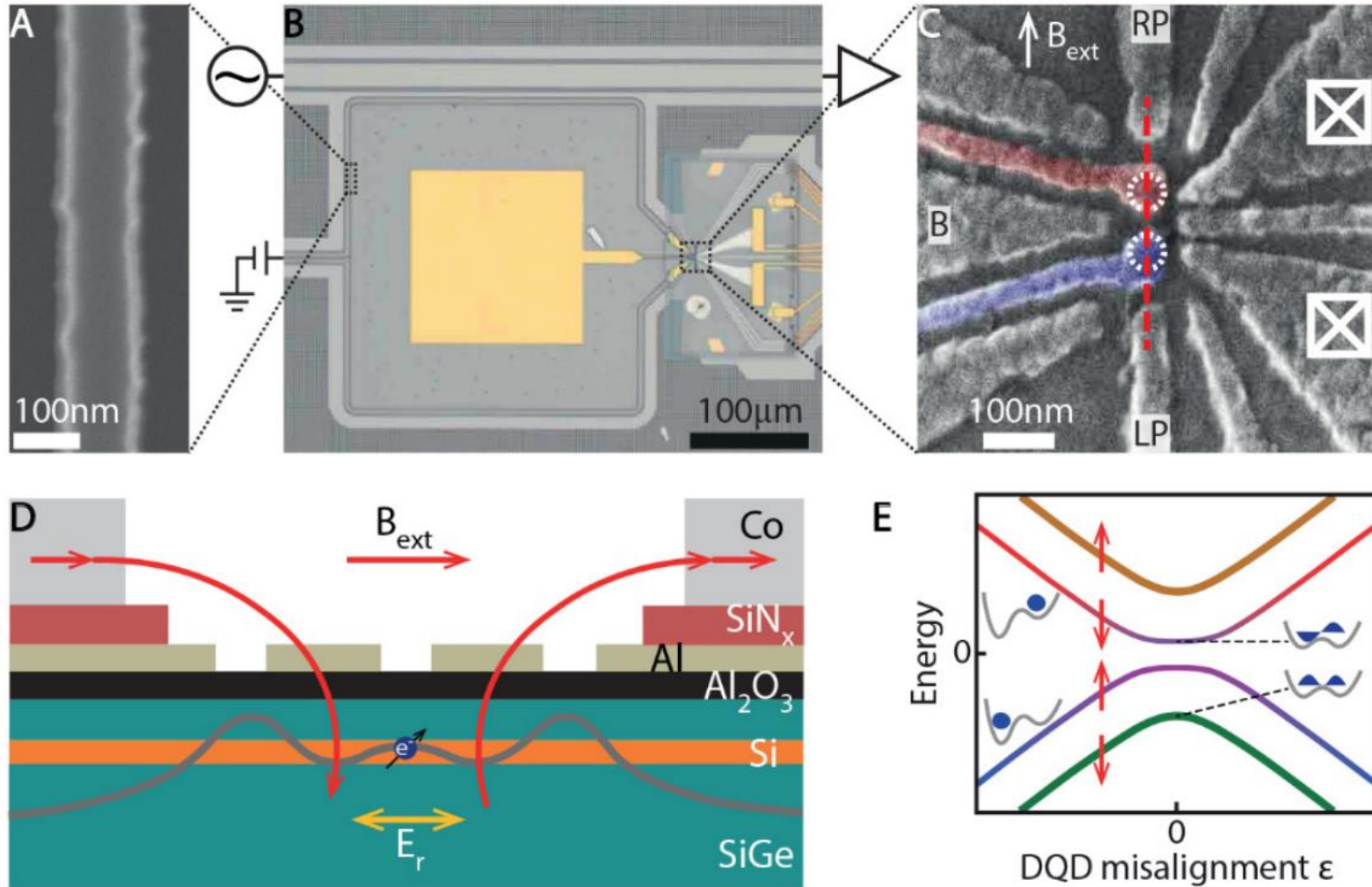

Science 09 Mar 2018:
Vol. 359, Issue 6380, pp. 1123-1127

Kinetic inductance, high-Z resonators

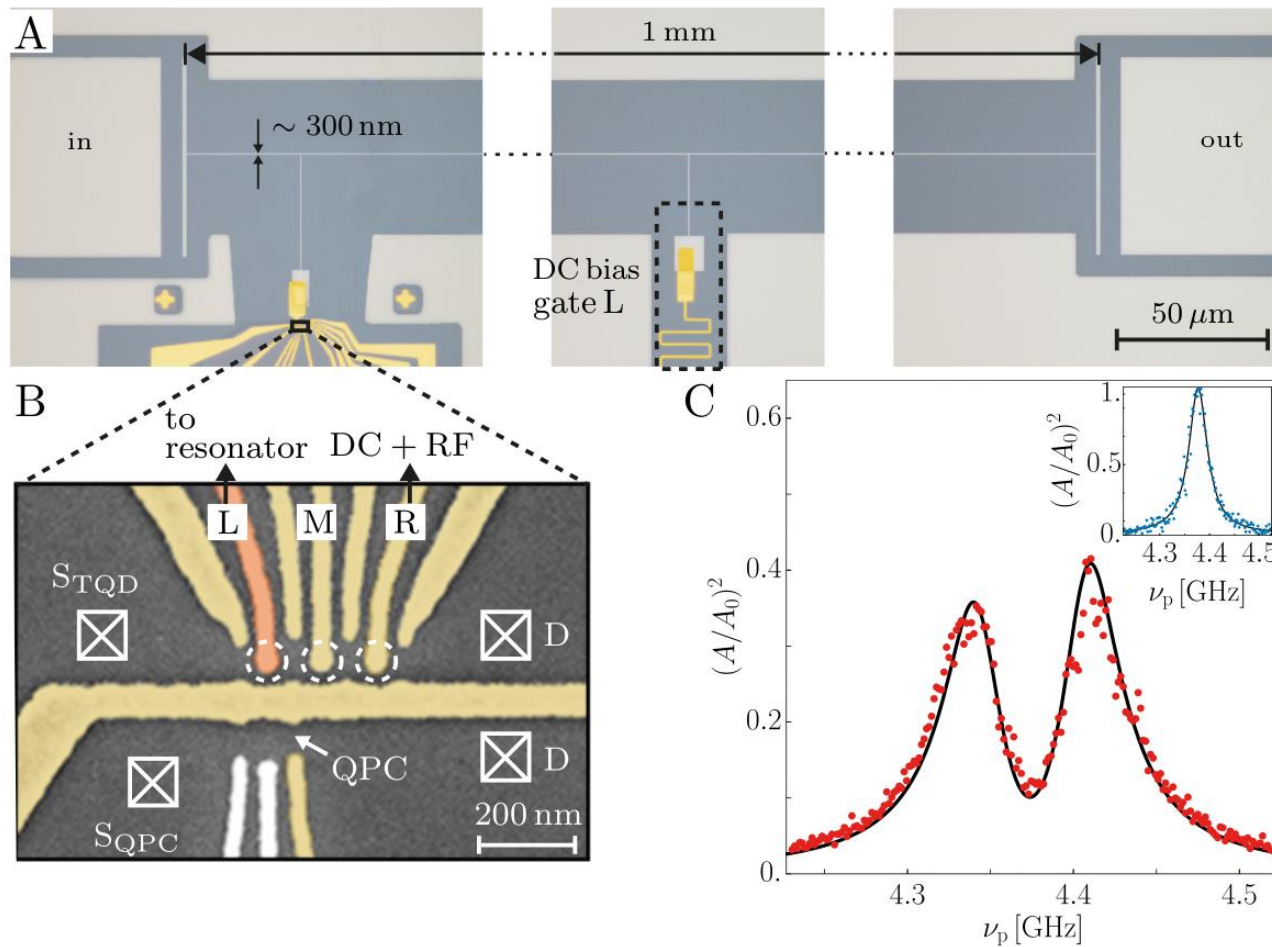- Realization in CPW geometry
 - Thin, narrow center conductor (300 nm, NbTiN)
 - $Z = 1.3 \text{ k}\Omega$




Nature **560**, 179–184 (2018)

Remarks

- Kinetic inductance detector
 - Distributed or lumped


- 20k pixels

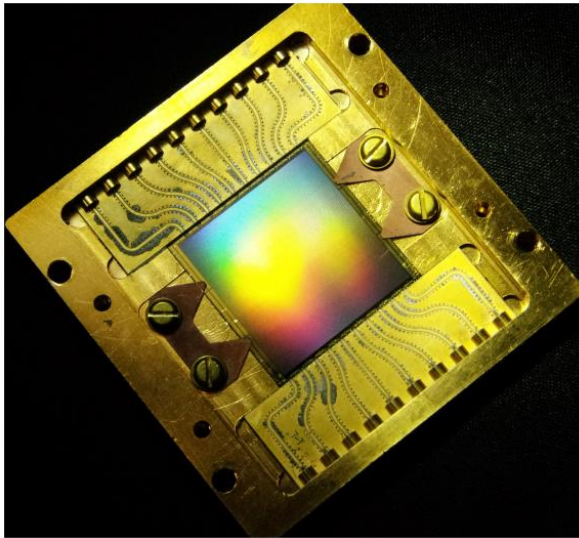

http://web.physics.ucsb.edu/~bmazin/Papers/szypryt_dissertation.pdf





$\lambda/4$ CPW resonator

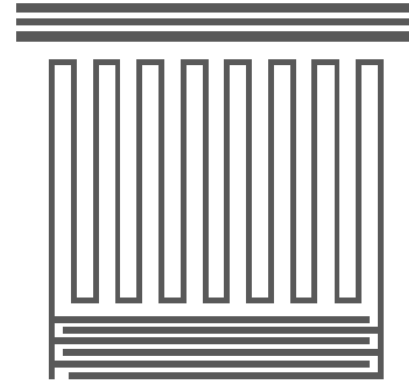


Lumped Element Kinetic Inductance Detector

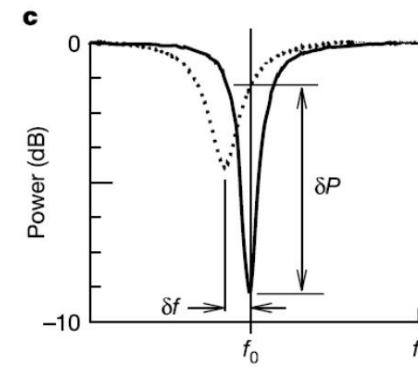
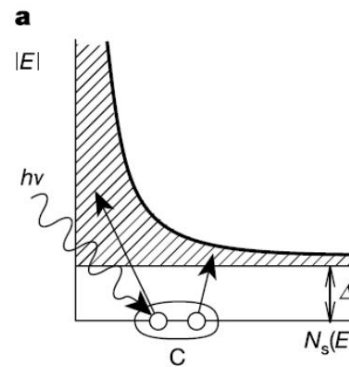
Journal of Low Temperature Physics 167 (3-4), 292-304



- Off-chip resonator: stub tuner

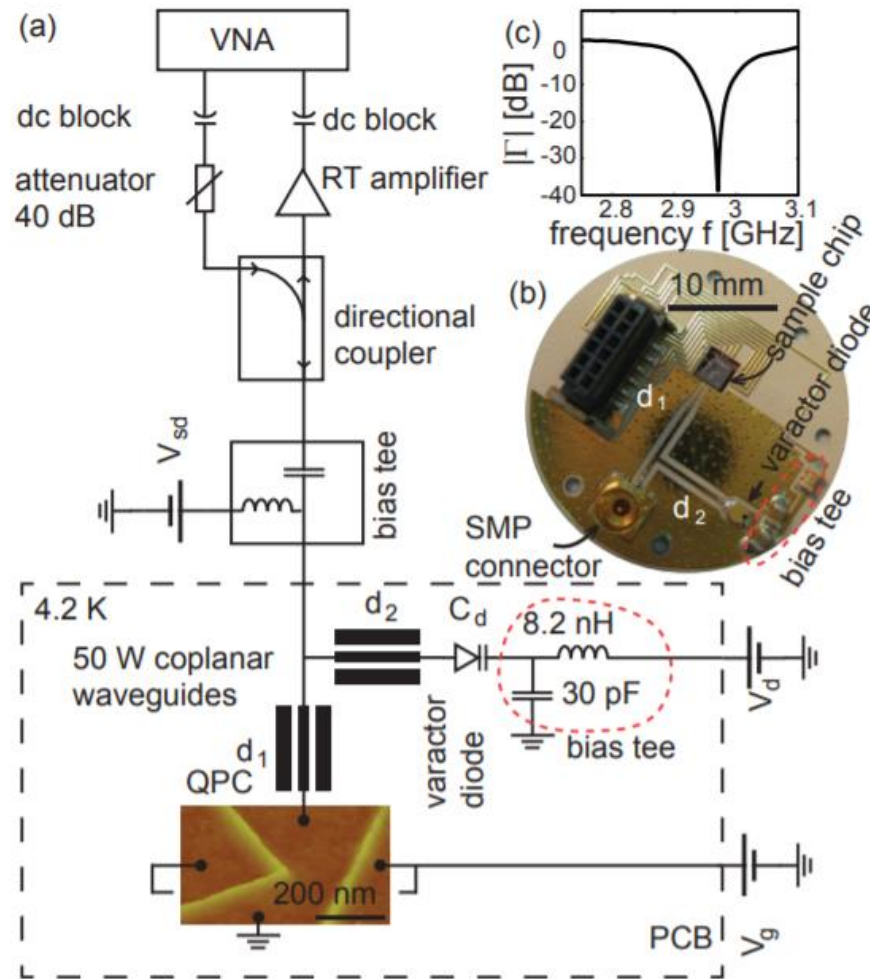


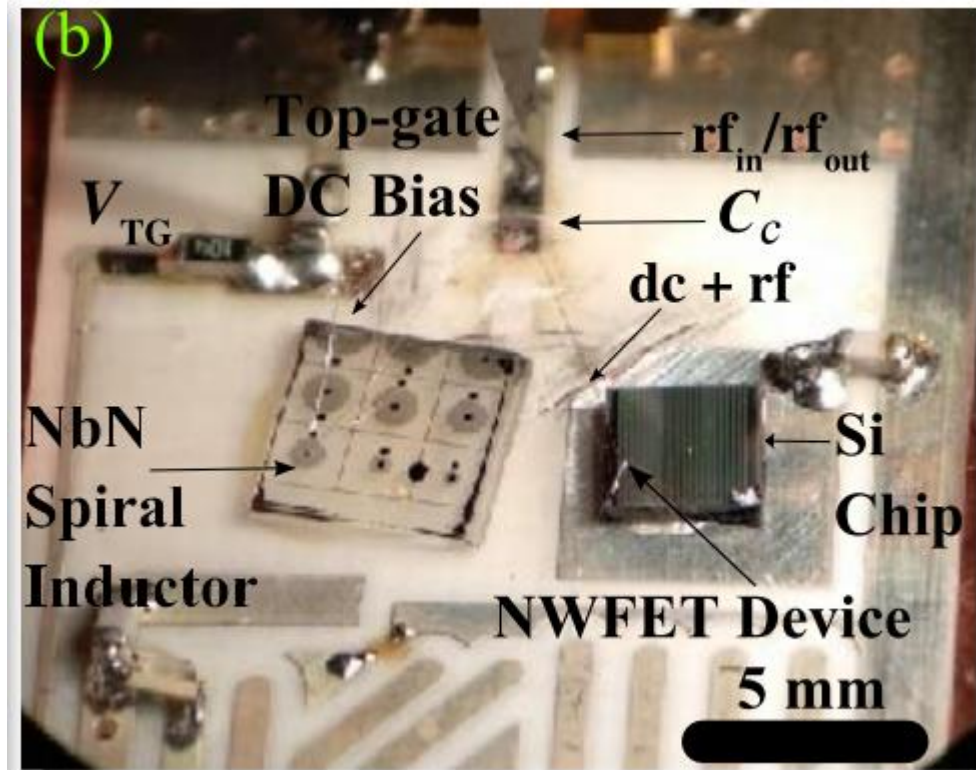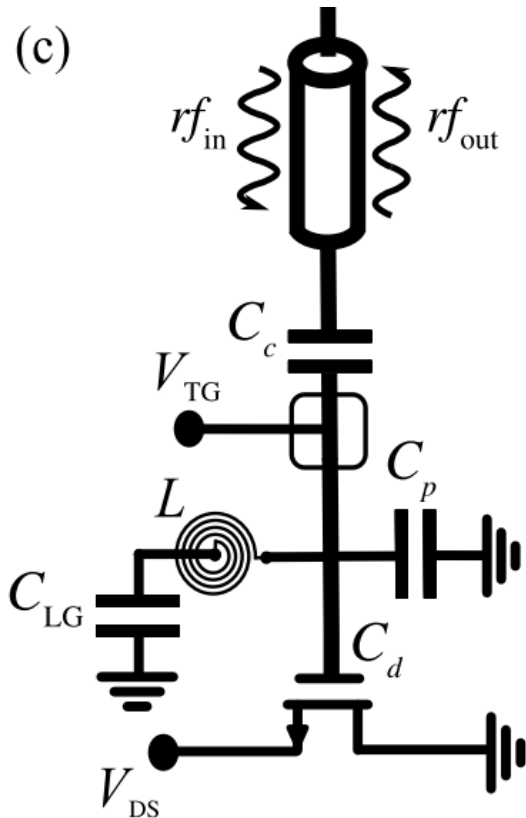- Off-chip resonator: SC meander inductor



Many-qubit architecture

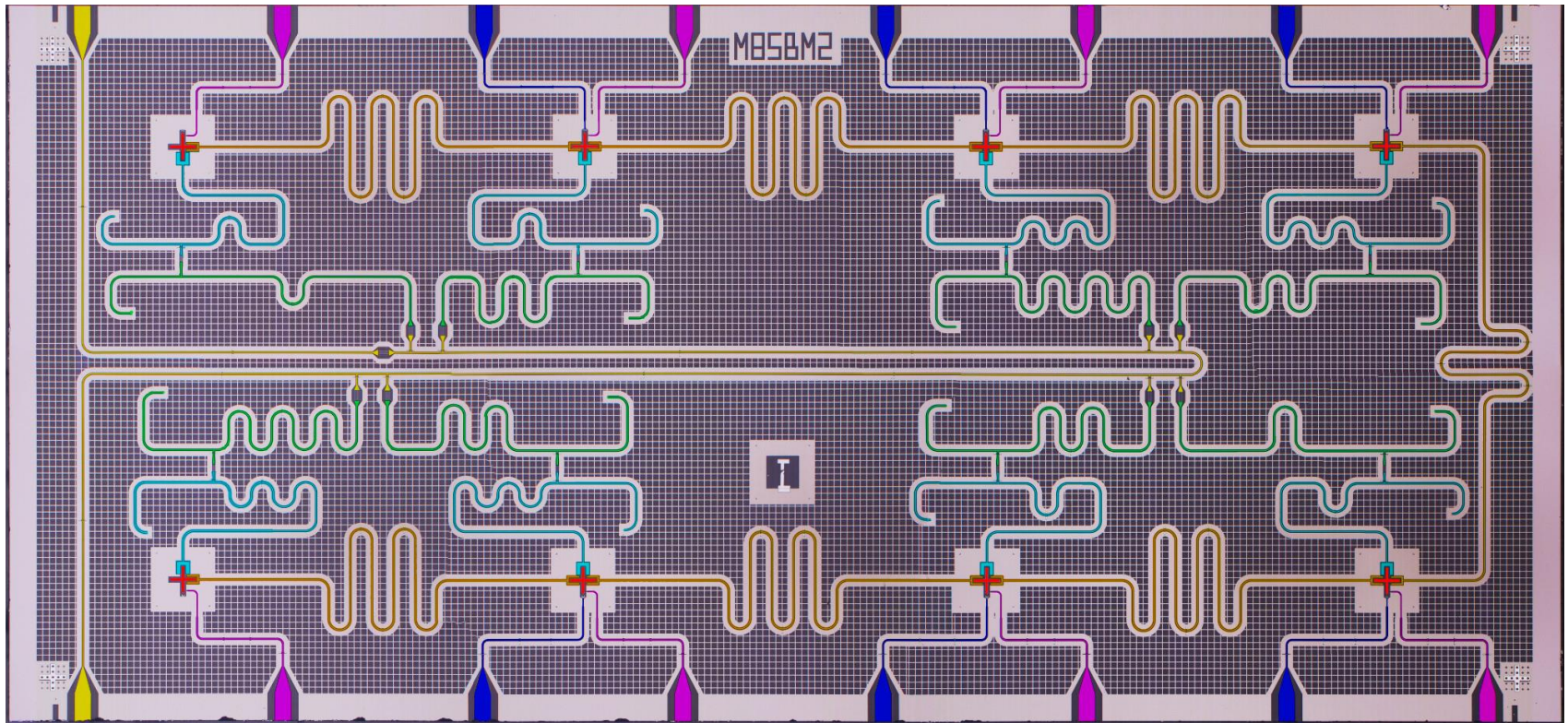- SC resonator for/as
 - Qubit read-out
 - Quantum bus
 - Purcell filter



ETH, <https://qt.eu/discover/technology/>